

The background of the slide features a large, faint, light blue circular seal of Yonsei University. The seal contains the university's name in English ("YONSEI UNIVERSITY") and Korean ("연세대학교"), the founding year "1885", and a central shield with a book and a torch.


# High-Speed Serial Interface Circuits and Systems

## Lecture 9: Tx Finite Impulse Response (FIR) Equalizer

Woo-Young Choi


Dept. of Electrical and Electronic Engineering  
Yonsei University

# Tx FIR

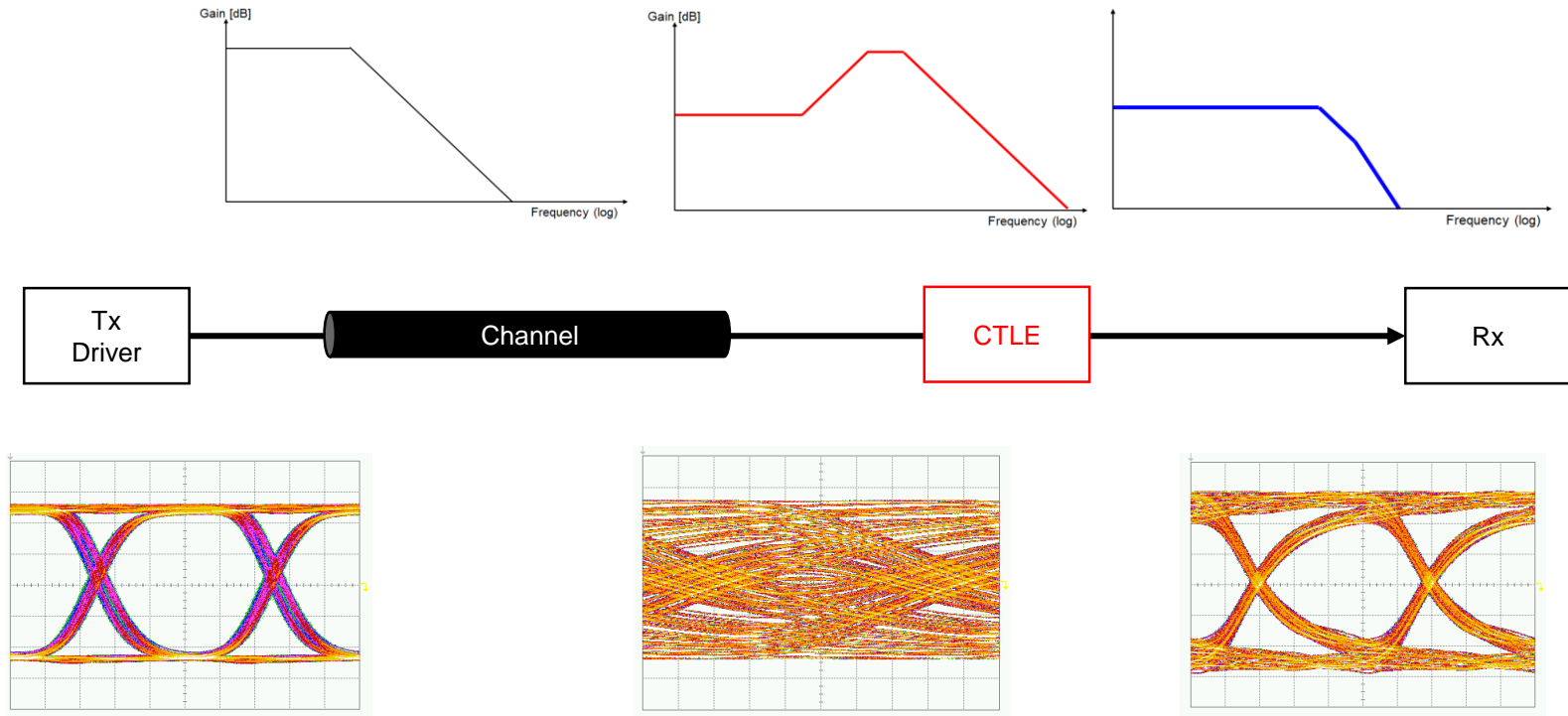

# Tx FIR

## CTLE

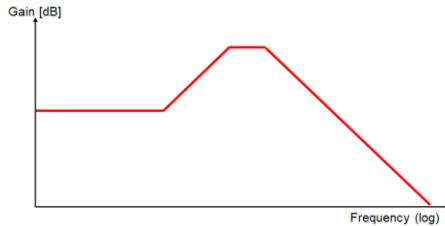


Discrete Time Domain Implementation?

s-domain analysis (CT) vs z-domain analysis (DT)

Bilinear transformation of s-domain filter into z-domain

$$(T: \text{Unit Interval}) \quad z = e^{sT} \sim \frac{1 + \frac{sT}{2}}{1 - \frac{sT}{2}} \quad s \sim \frac{2}{T} \frac{z-1}{z+1} = \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}}$$

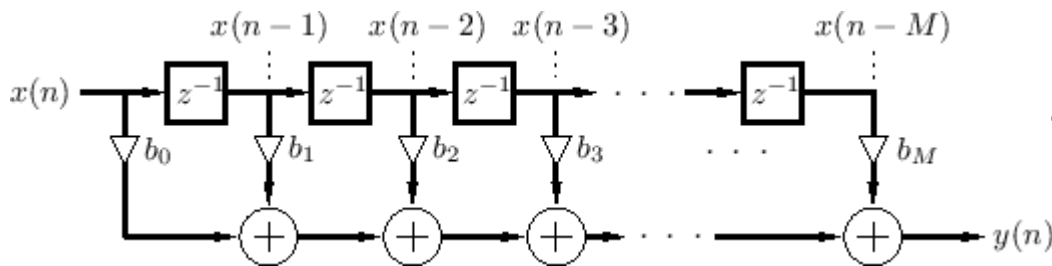➔ Possible to approximately implement with Finite-Impulse Response (FIR)





Tapped and Delay

Simple to implement

No stability problem (No feedback)

# Tx FIR


## FIR

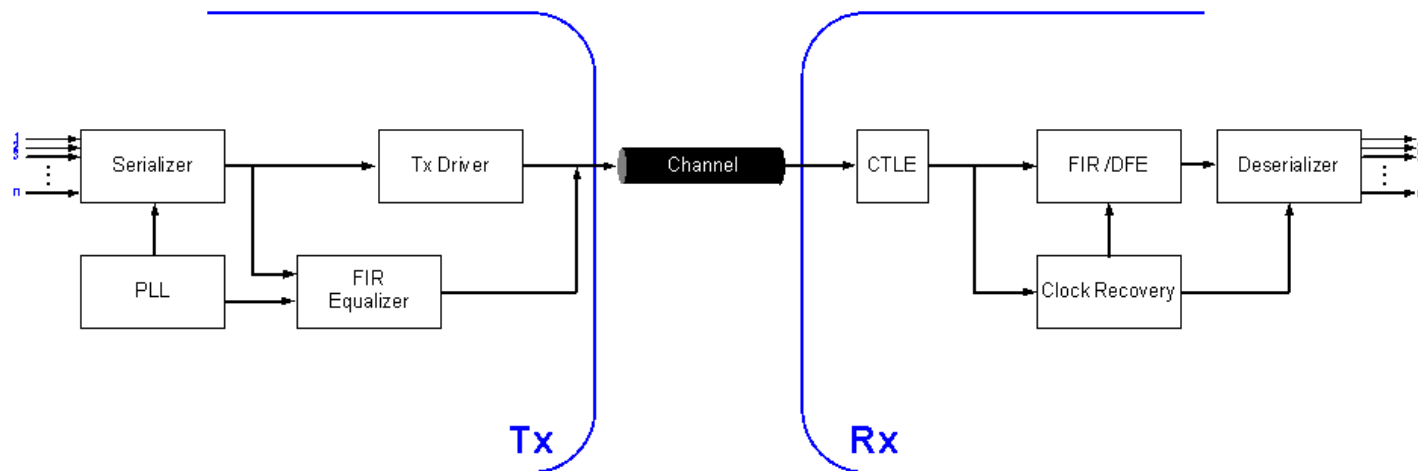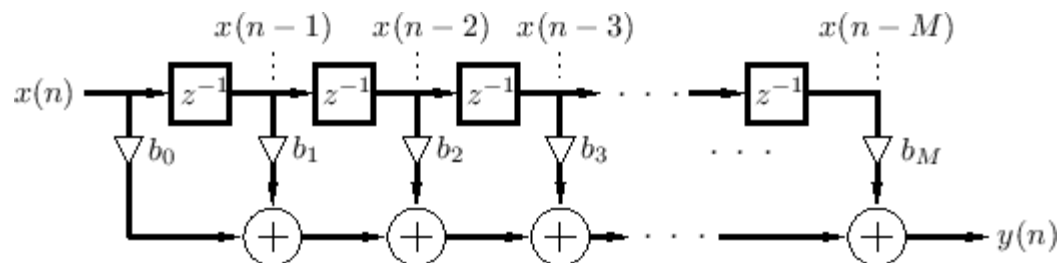

Tx FIR much easier to implement



# Tx FIR

FIR coefficient determination

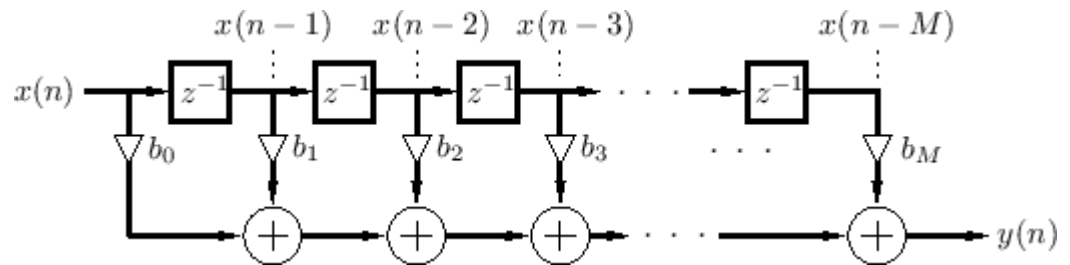


CTLE:


Frequency-domain analysis

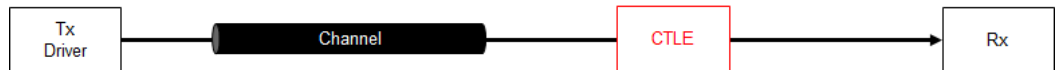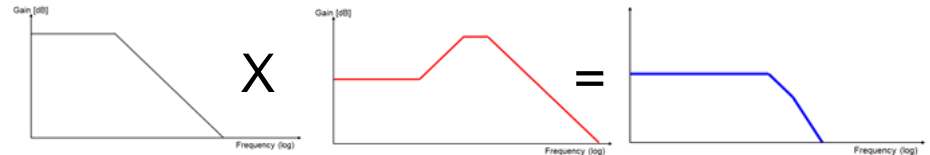


Time-domain analysis for FIR

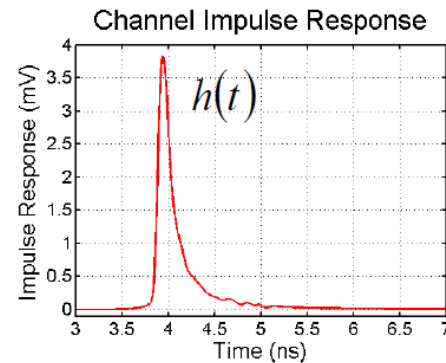


# Tx FIR

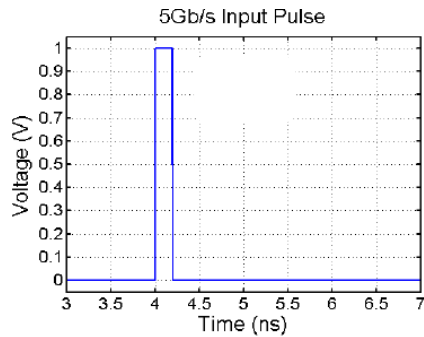

\*

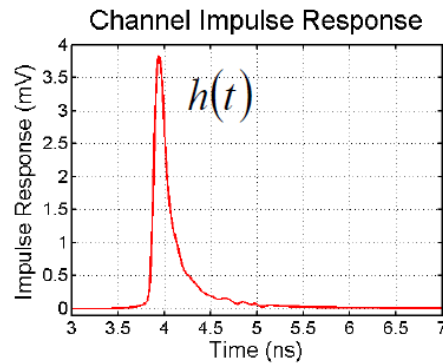


=


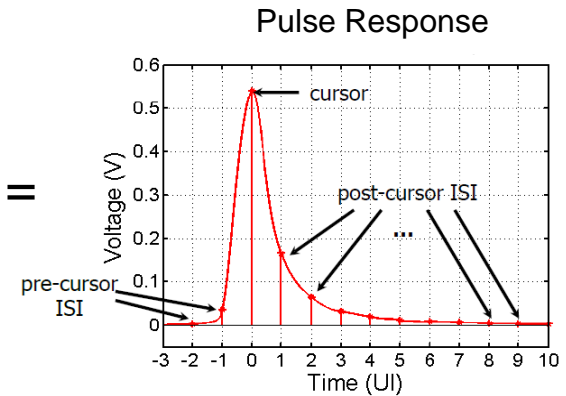


Random  
Bit Sequence

\*

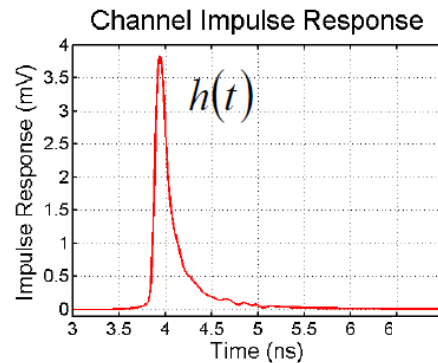


=

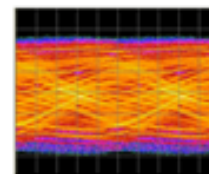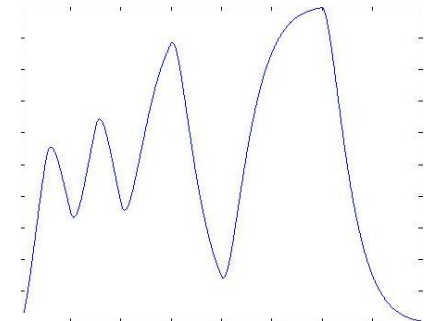


Inter-Symbol Interference

# Tx FIR

FIR coefficient determination


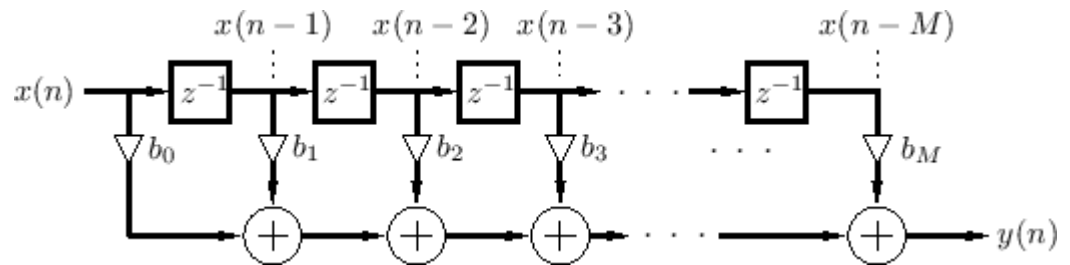


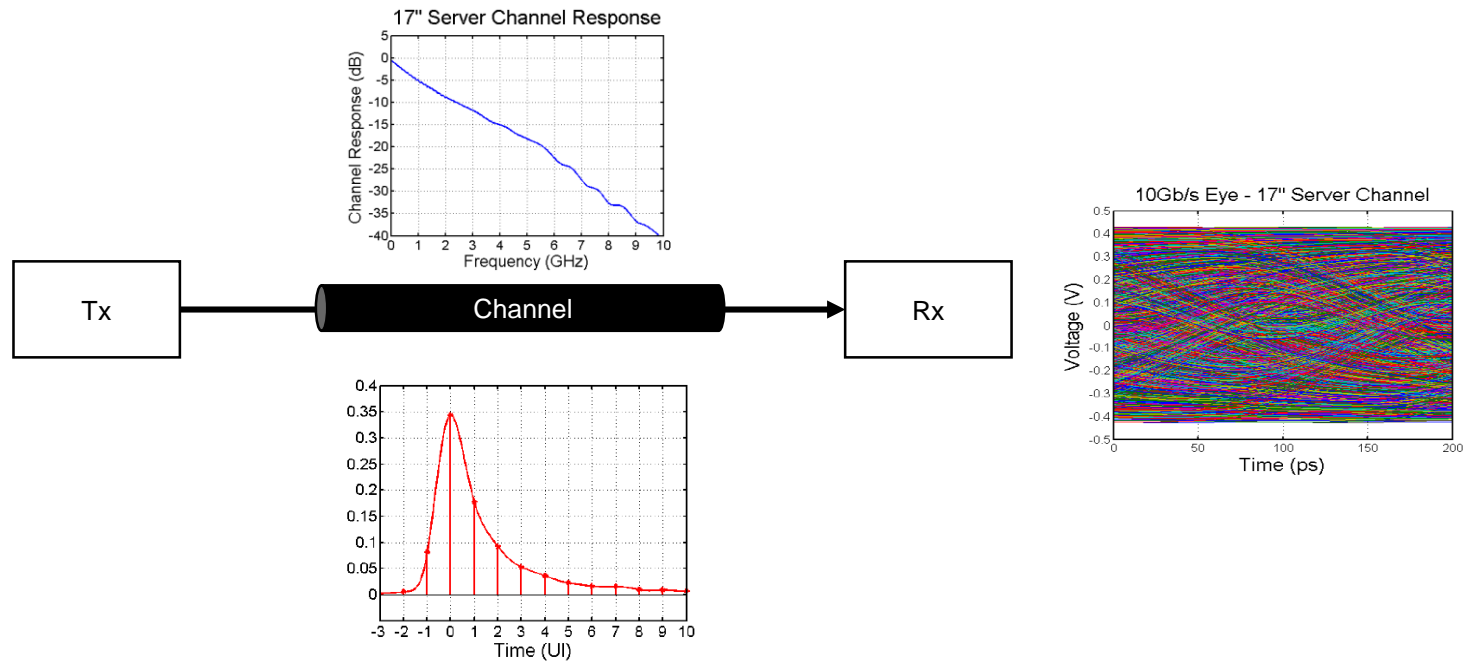Example (From Prof. Palermo of TAMU class notes)



# Tx FIR

Use 3-tap FIR for simplicity

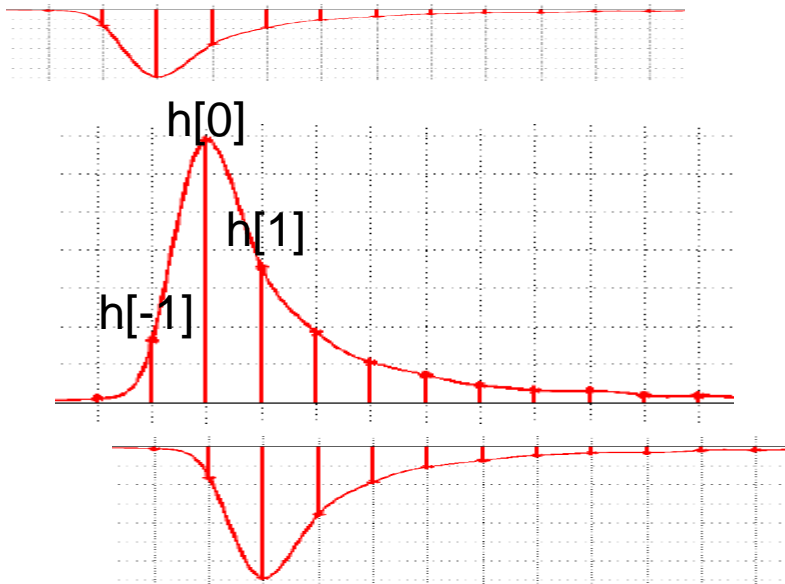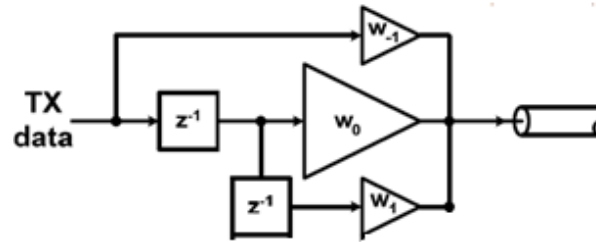

$$w_{-1}h[0] + w_0h[-1] + w_1h[-2] = 0$$





$$w_{-1}h[1] + w_0h[0] + w_1h[-1] = 1$$

$$w_{-1}h[2] + w_0h[1] + w_1h[0] = 0$$





$$\begin{bmatrix} w_{-1} \\ w_0 \\ w_1 \end{bmatrix} \sim \begin{bmatrix} -0.13 \\ 0.60 \\ -0.27 \end{bmatrix}$$





# Tx FIR

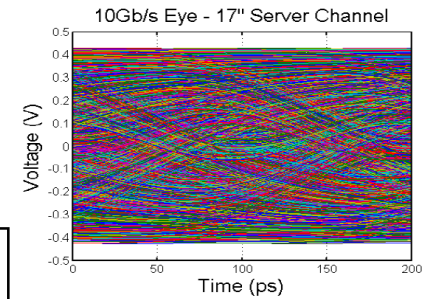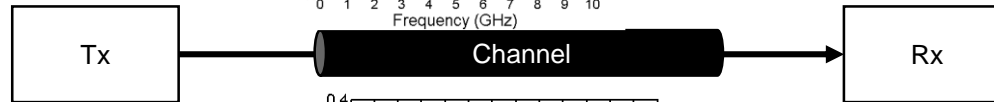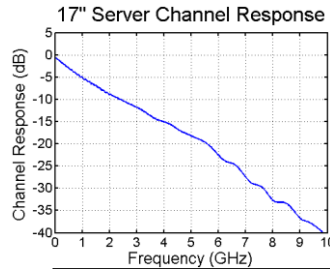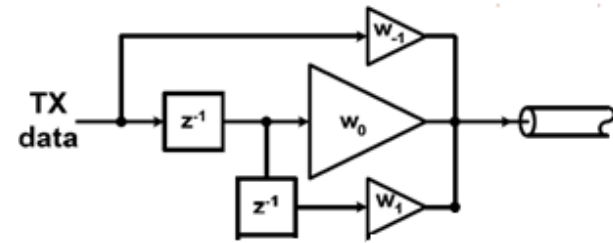
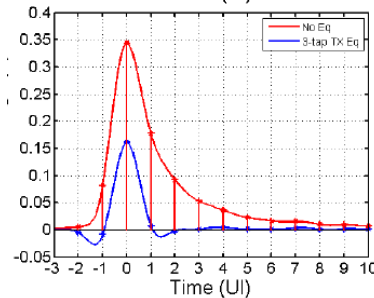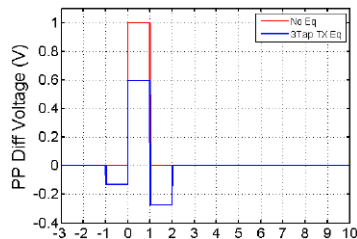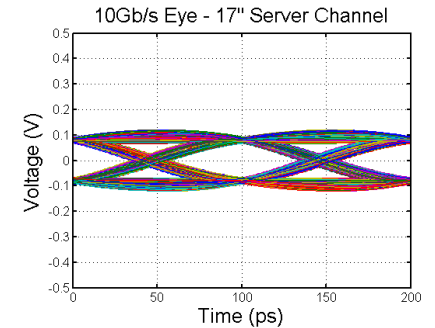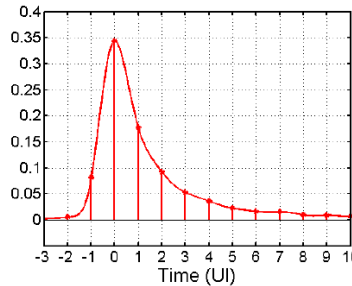
$$\begin{bmatrix} w_{-1} \\ w_0 \\ w_1 \end{bmatrix} = \begin{bmatrix} -0.13 \\ 0.60 \\ -0.27 \end{bmatrix}$$




# Tx FIR

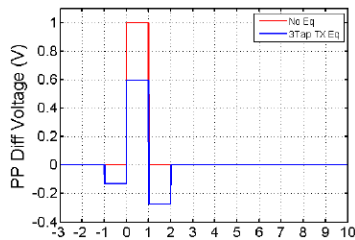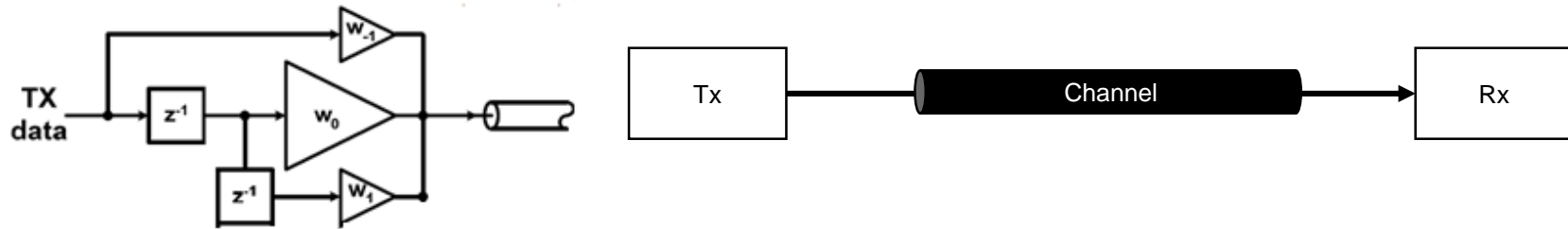

$$\begin{bmatrix} w_{-1} \\ w_0 \\ w_1 \end{bmatrix} = \begin{bmatrix} -0.13 \\ 0.60 \\ -0.27 \end{bmatrix}$$

$$W[z] = -0.13 + 0.60z^{-1} - 0.27z^{-2}$$

Corresponding frequency response?

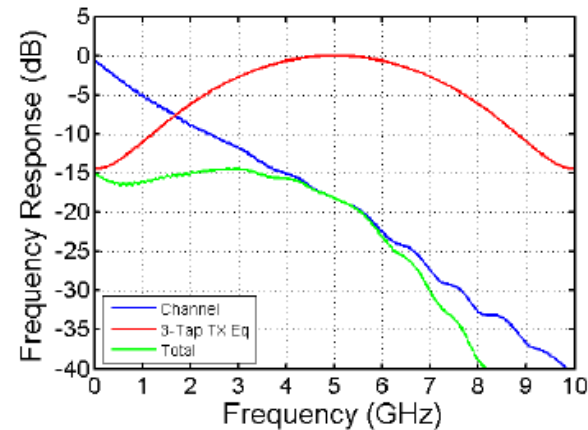

FIR → High Pass Filter

$$z = e^{sT} \implies e^{j2\pi fT}$$


Low Frequency Response ( $f = 0$ )

$$z = 1 \quad H(f = 0) = 0.2 \implies -14dB$$

Nyquist Frequency Response  $\left(f = \frac{1}{2T}\right)$

$$z = -1 \quad H\left(f = \frac{1}{2T}\right) = -1 \quad |H| = 0dB$$


# Tx FIR

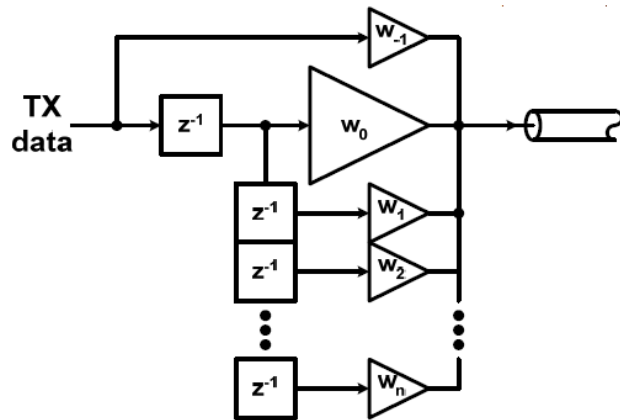

Tap coefficients?



Minimum Mean-Square Error (MMSE) algorithm  
for pre-, post-cursor reduction with the given tap number

# Tx FIR

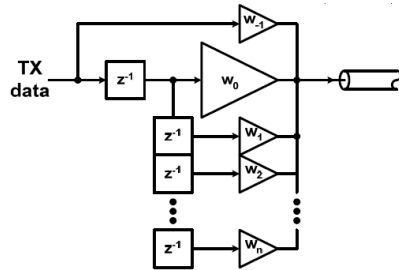

How many taps?

(From Prof. Palermo of TAMU class notes)

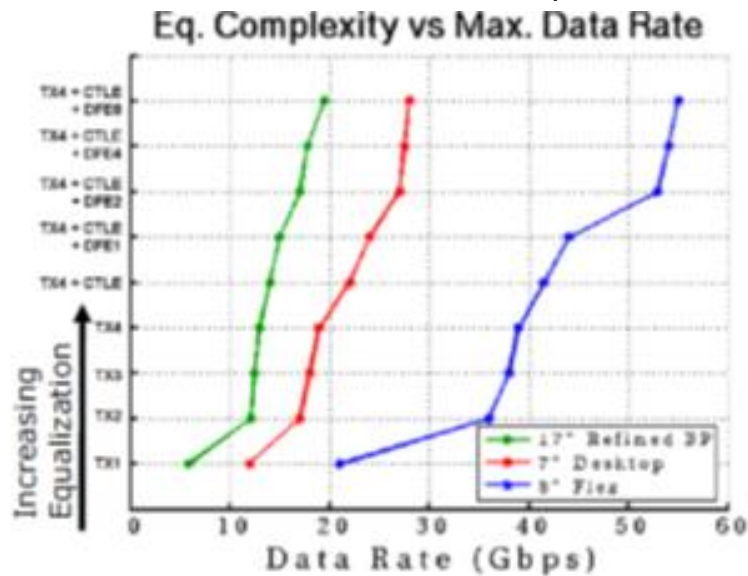
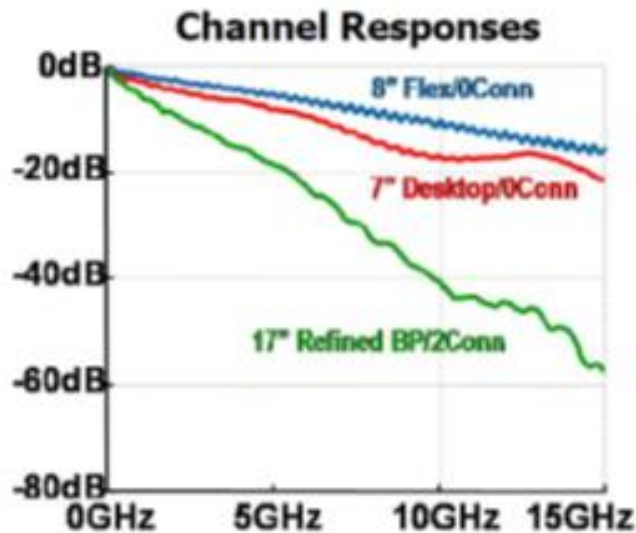


3-tap FIR gives significant performance enhancement

Tx FIR → CTLE → Decision-Feedback Equalizer (DFE)
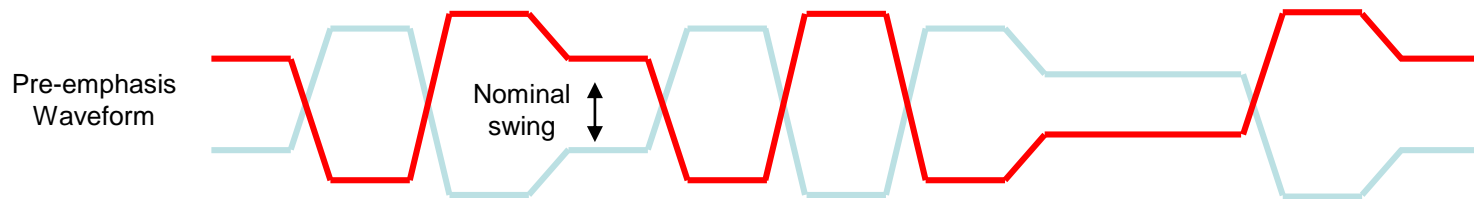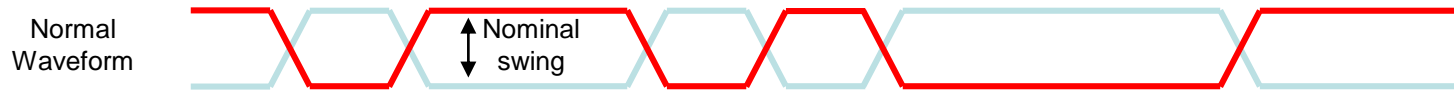
# Tx FIR

2-Tap FIR (main and 1<sup>st</sup> post-cursor) also called Pre-/De-Emphasis




Pre-emphasis: Enhance high-frequency components



De-emphasis: Reduce low-frequency components
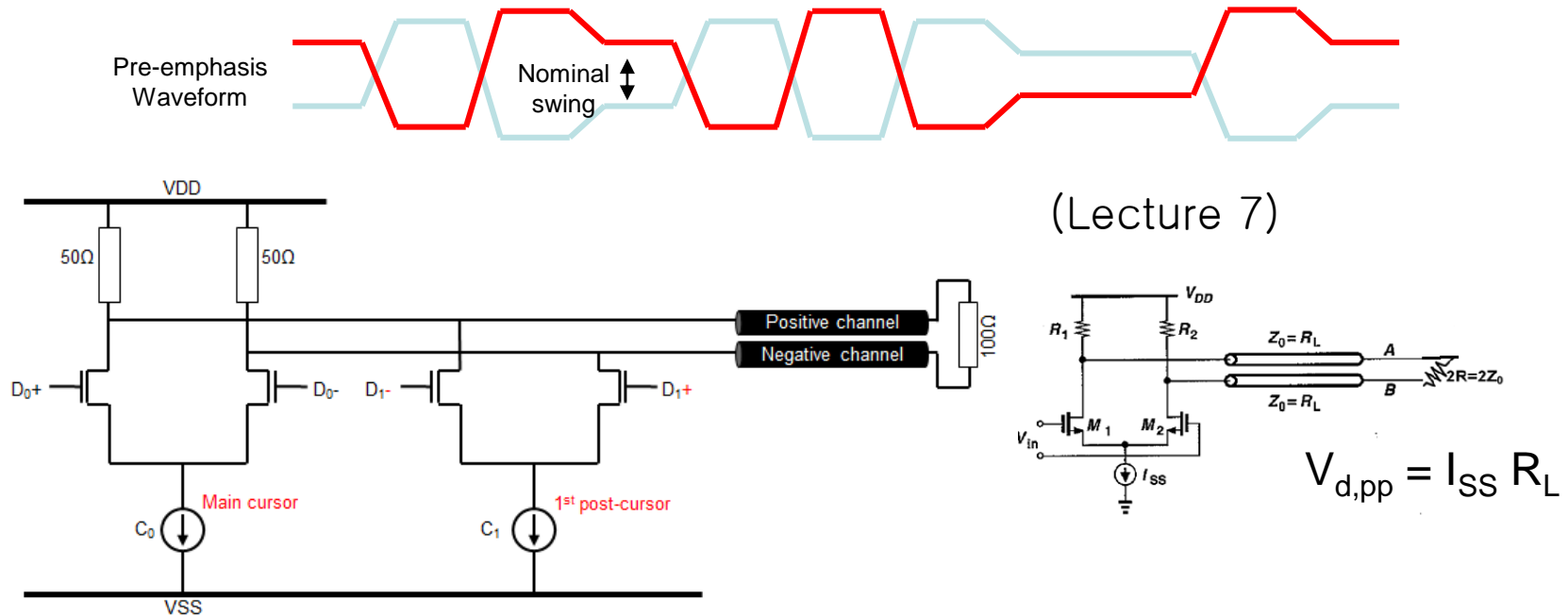
# Tx FIR

- Tx FIR can be easily implemented with CML drivers



- $D_1 \neq D_0$   $V_{d,pp} = (C_0 + C_1) \times 50$
- $D_1 = D_0$   $V_{d,pp} = (C_0 - C_1) \times 50$

More taps can be implemented by adding parallel CML drivers with proper polarity

# Tx FIR

Homework: (Due on 11/16)

An FIR filter has the z-domain system function given as  $H(z) = a + b z^{-1} + c z^{-2}$ .

- (a) Draw the block diagram for an NRZ transmitter equalizer implementing above system function. Your block diagram should contain only delay elements with delay  $T$ , the unit interval, and the drivers having the required gain.
- (b) Determine how much high-frequency peaking above equalizer provides at the Nyquist frequency ( $=1/2T$ ) compared to the DC gain. Use the linear scale.
- (c) Show the circuit schematic of an differential current-mode driver implementing above equalizer.