

# TX FIR Equalizer – CM mode

12 Gbps

**(Final Report)**

Muhammad Aldacher


# Outline

1. Background
2. Implementation
3. Schematics
4. Simulation Results
  - a) Pulse Response
  - b) Eye Diagram
  - c) Transient Waveforms

# Background


- "TX FIR equalization" is the technique in which a transmitter applies a Finite Impulse Response (FIR) filter to pre-distort the signal before sending it.
- This is to compensate for the distortions introduced by the transmission channel, thus improving signal quality at the receiver by mitigating intersymbol interference (ISI).

# Background

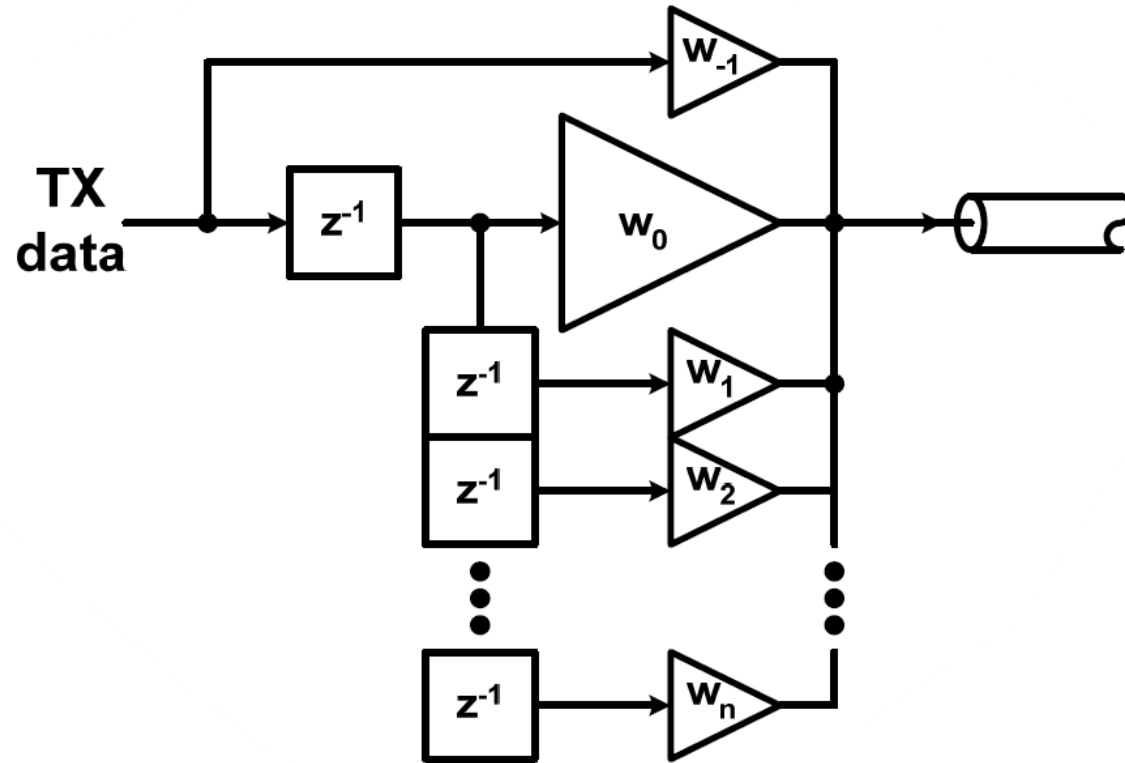


## Time Domain


Input Pulse w/ 3-tap TX Eq

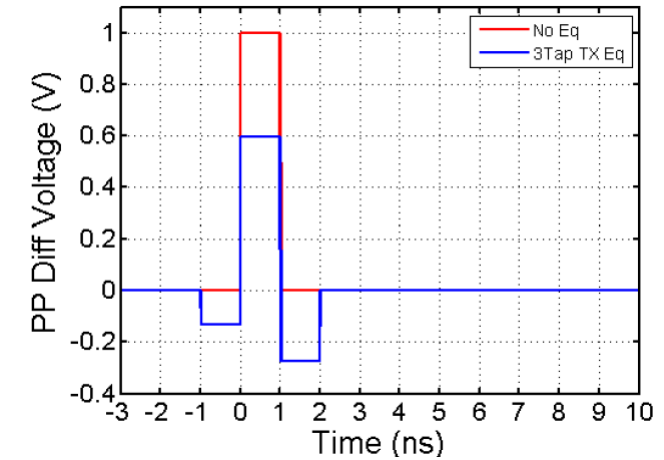


Output Pulse Response

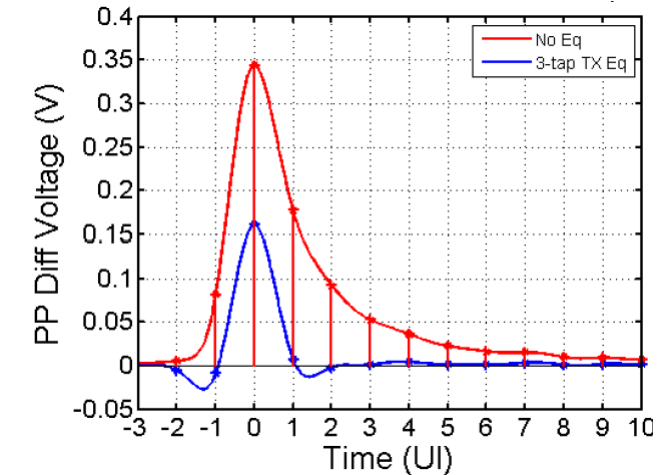

# Background

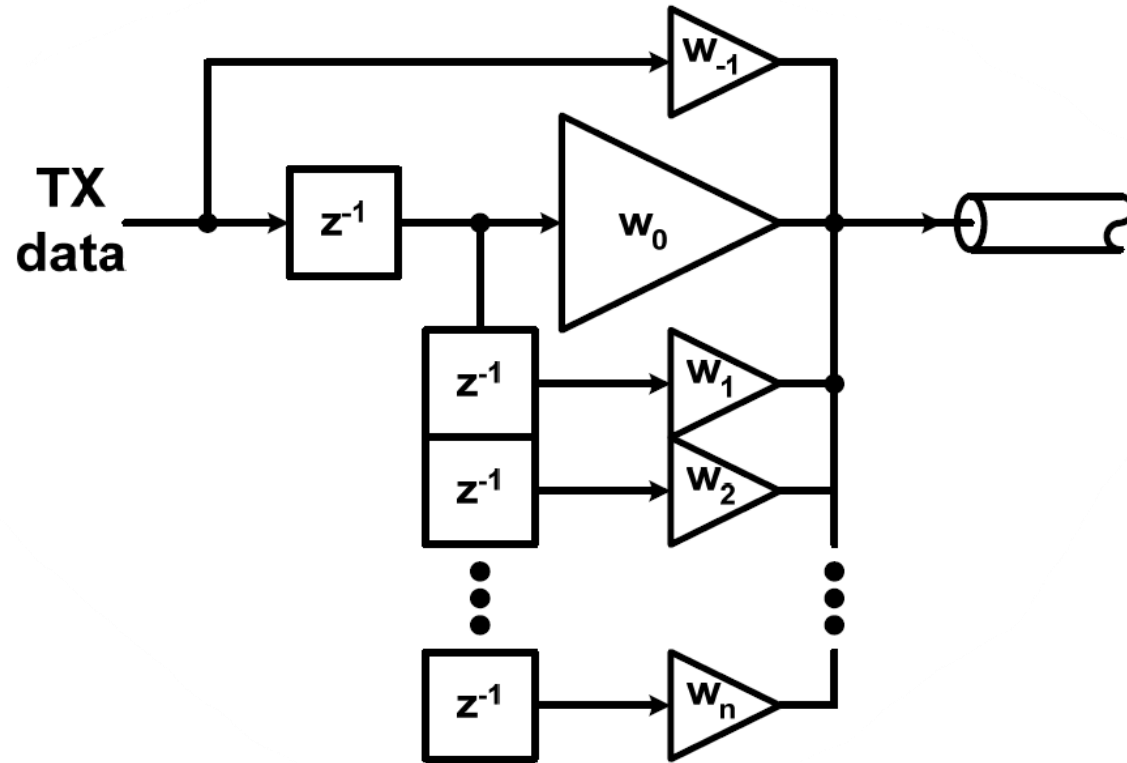


## Freq Domain

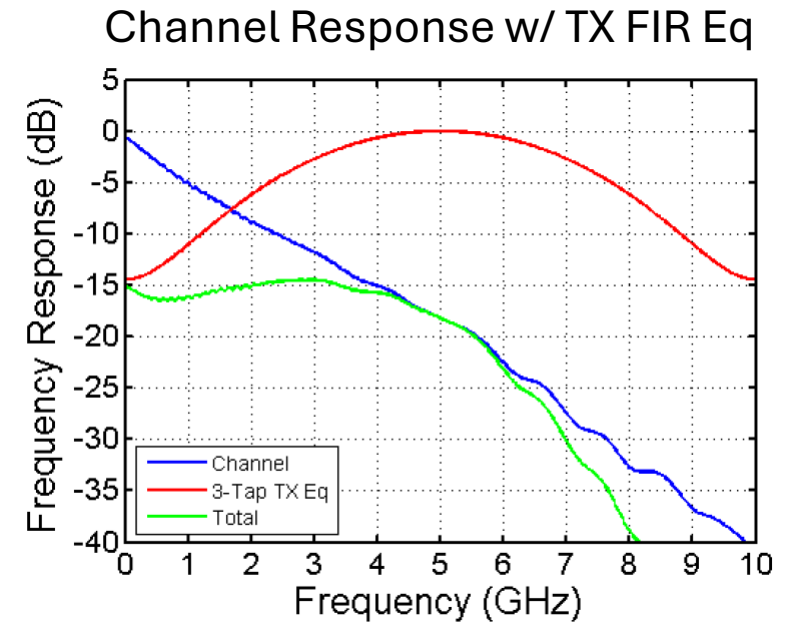


# Implementation

- For CML driver:

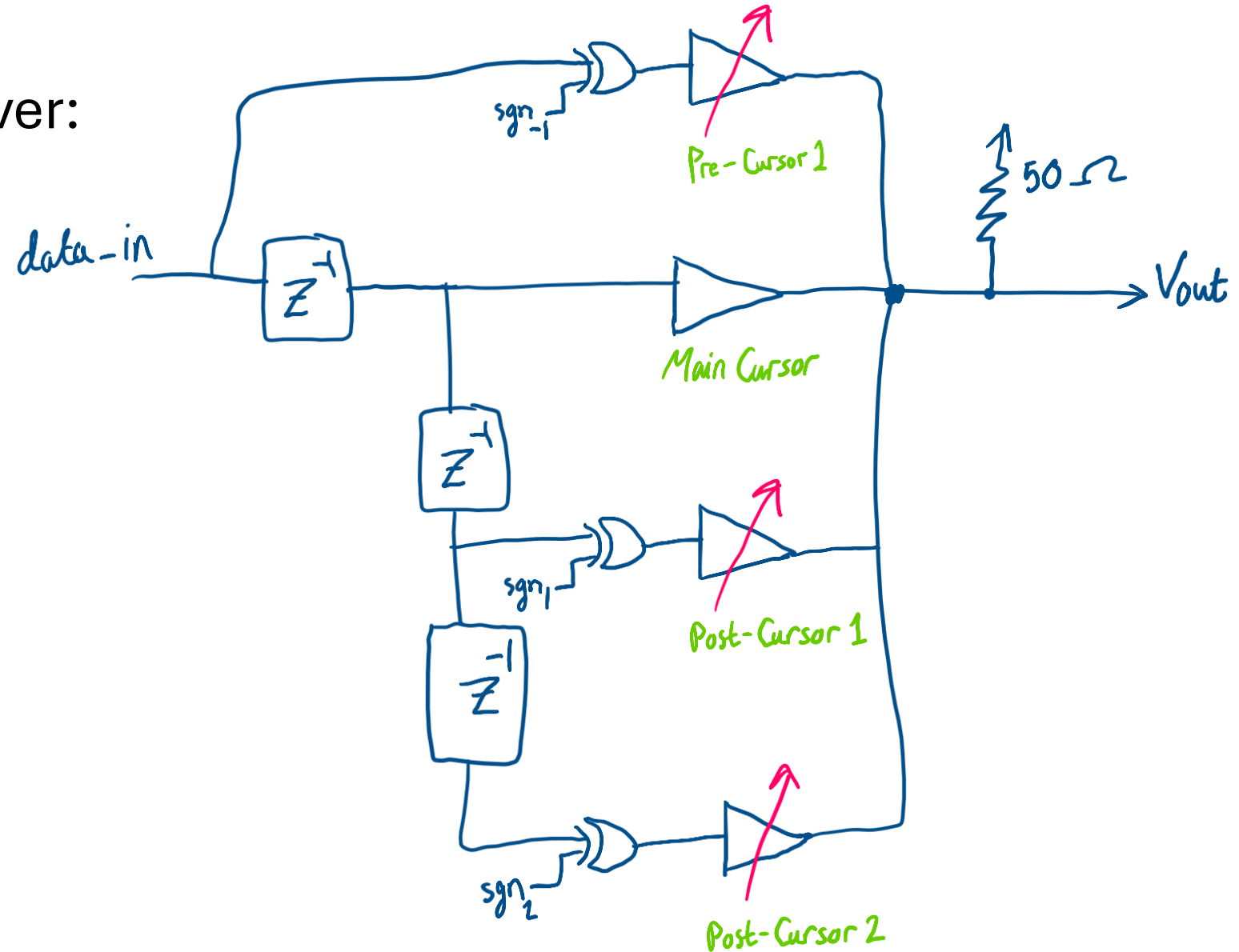


# Implementation

- For CML driver:

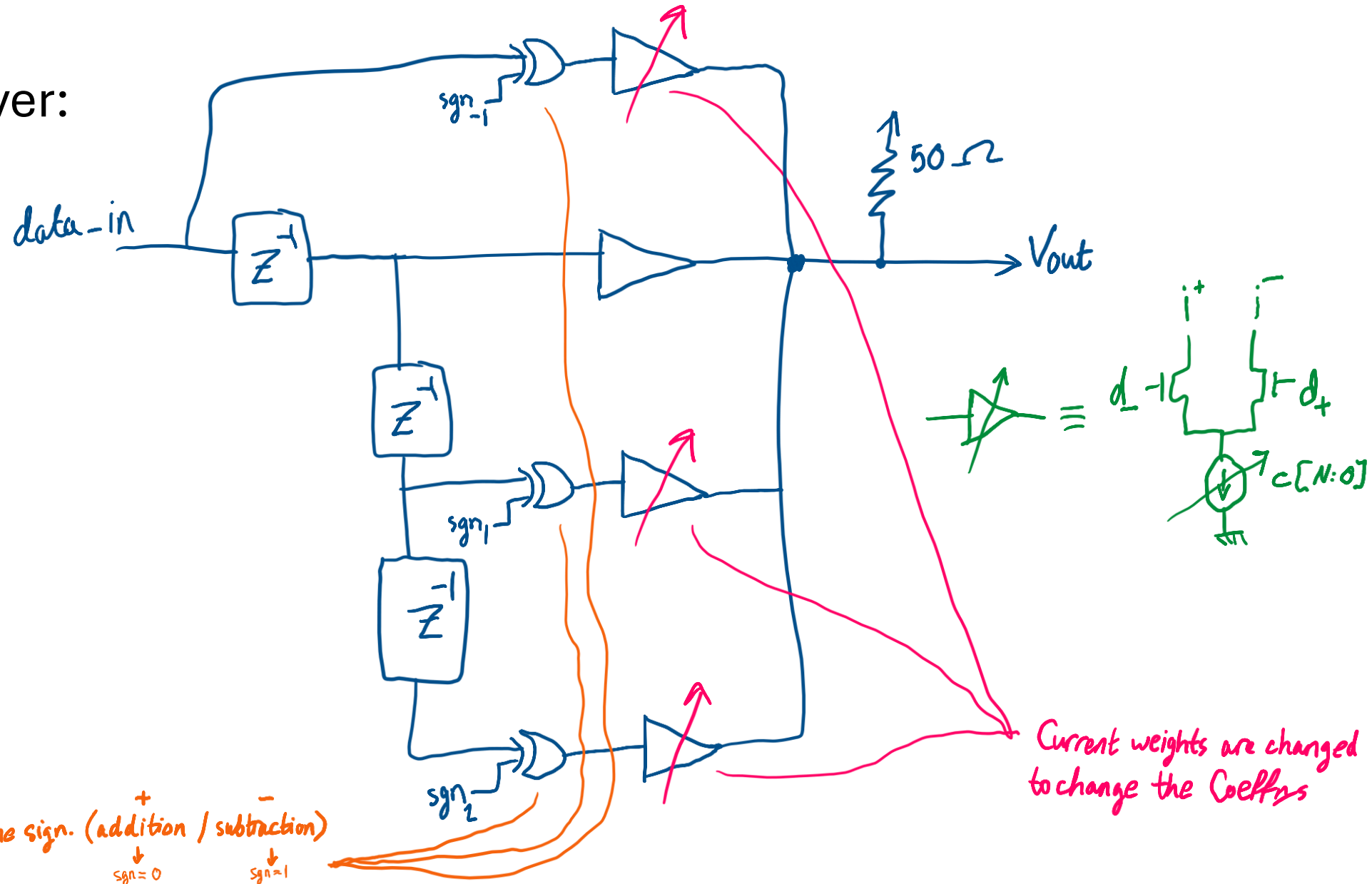

# Schematics

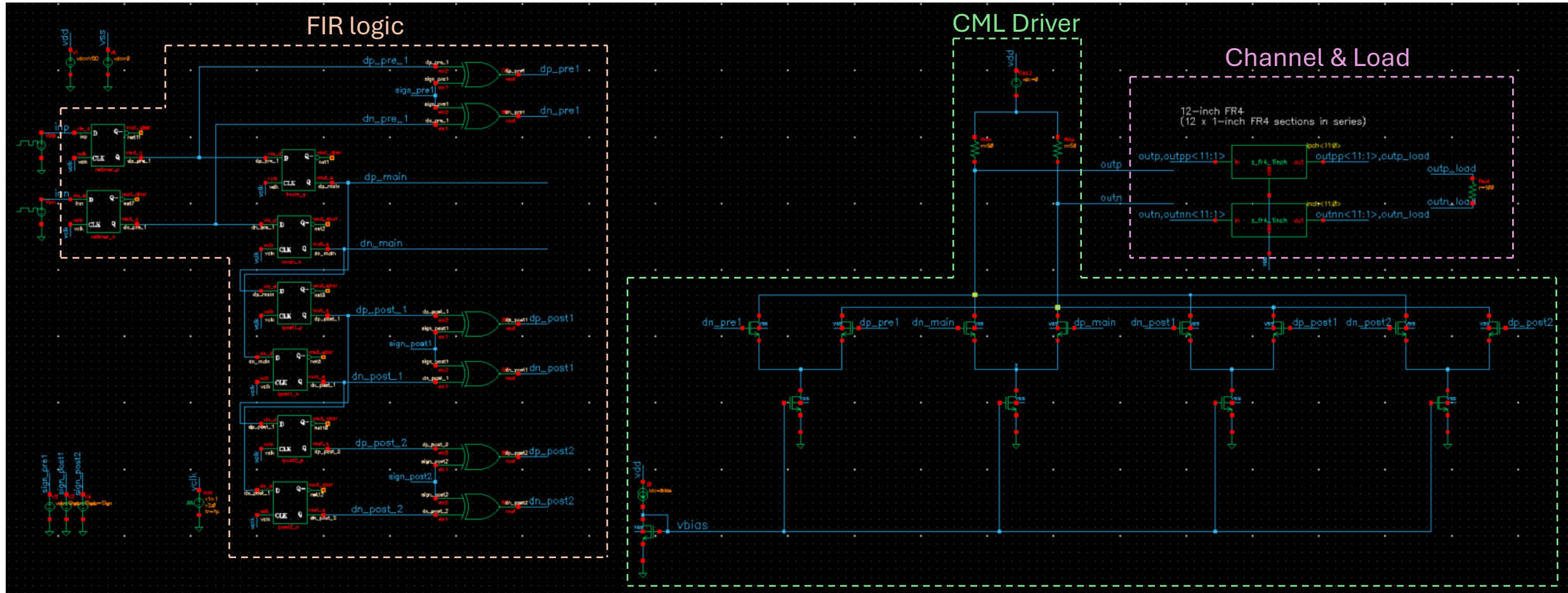




# Schematics

## A) FIR Logic:

12 Gb/s PRBS  
Inputs

12 GHz Clock

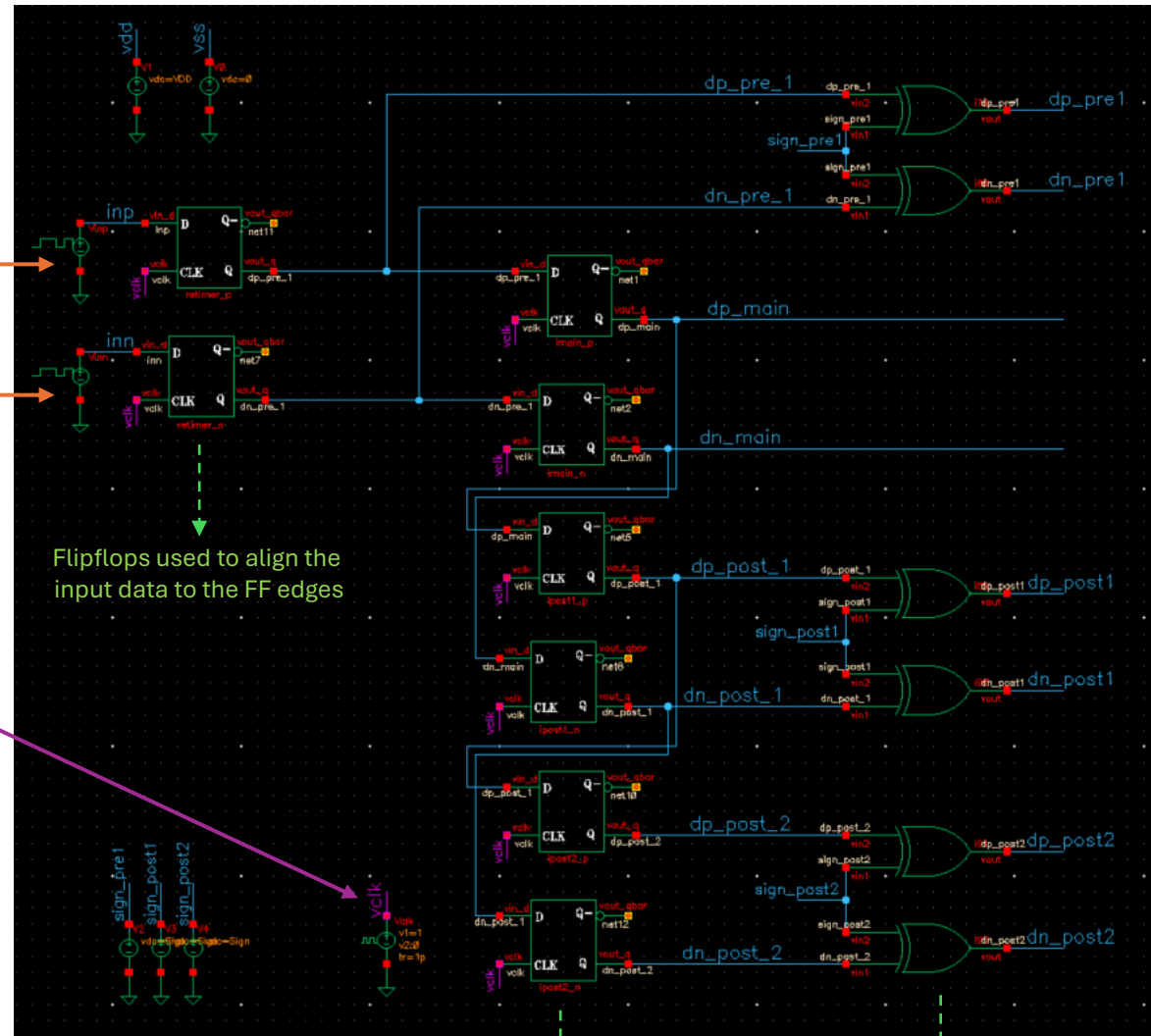

Flipflops used to align the  
input data to the FF edges

Flipflops used as delay cells

XOR gates used to apply the  
sign to the cursor taps

Pre-Cursor 1


Main-Cursor

Post-Cursor 1

Post-Cursor 2



# Schematics

## B) CML Driver:

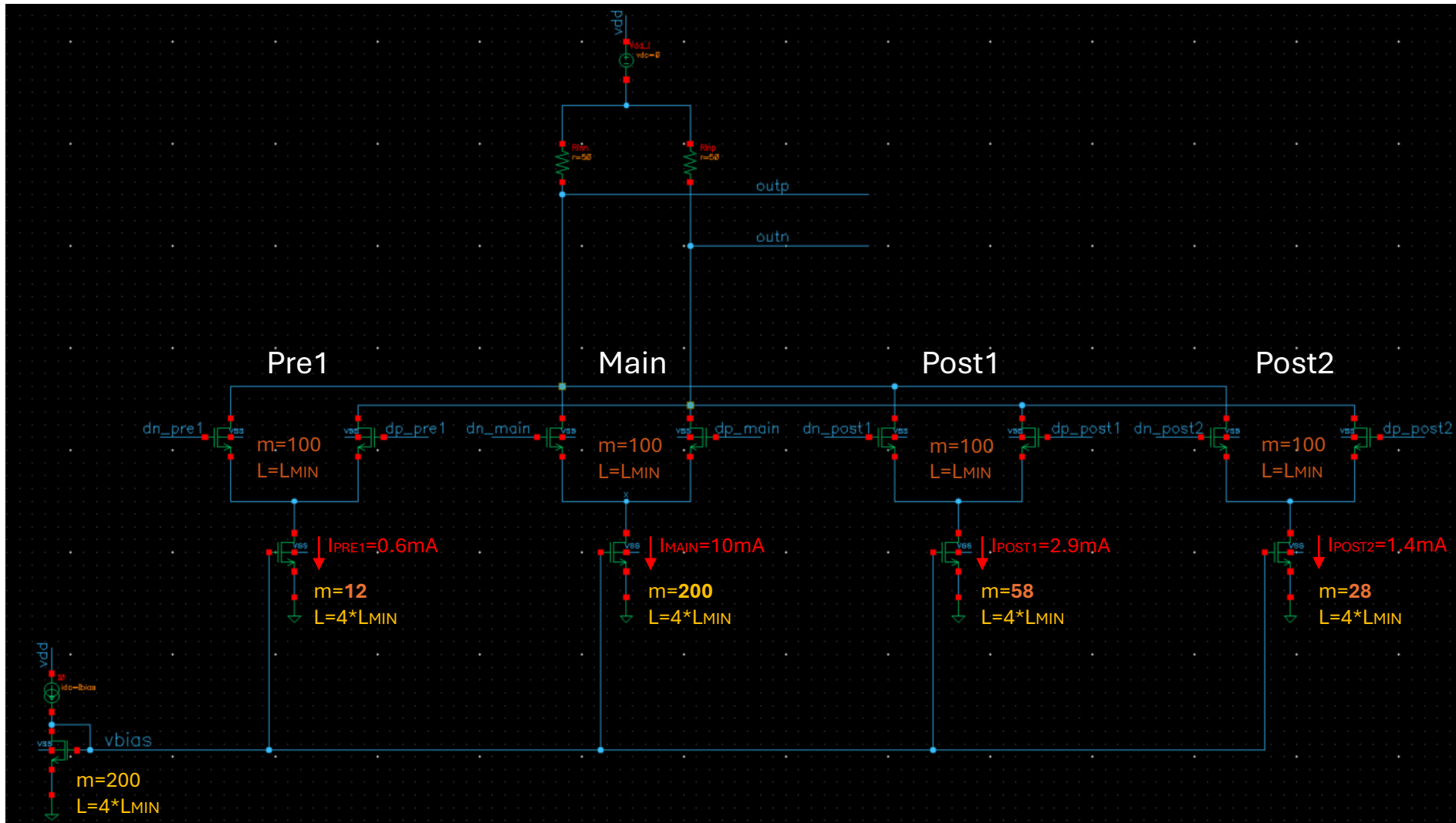

# Schematics


## C) Channel & Load:

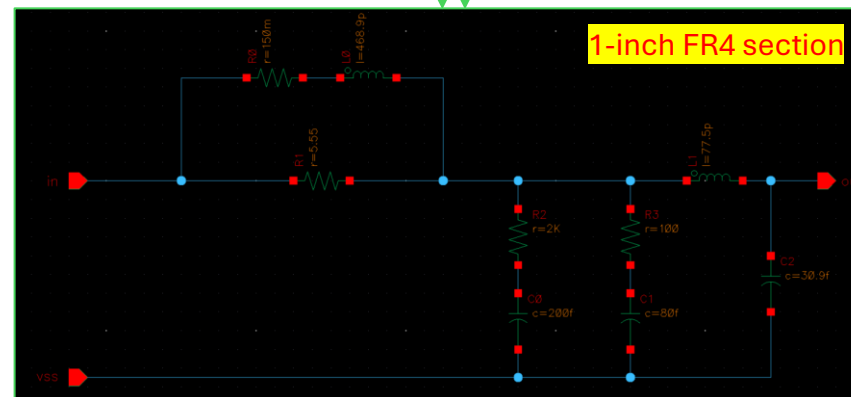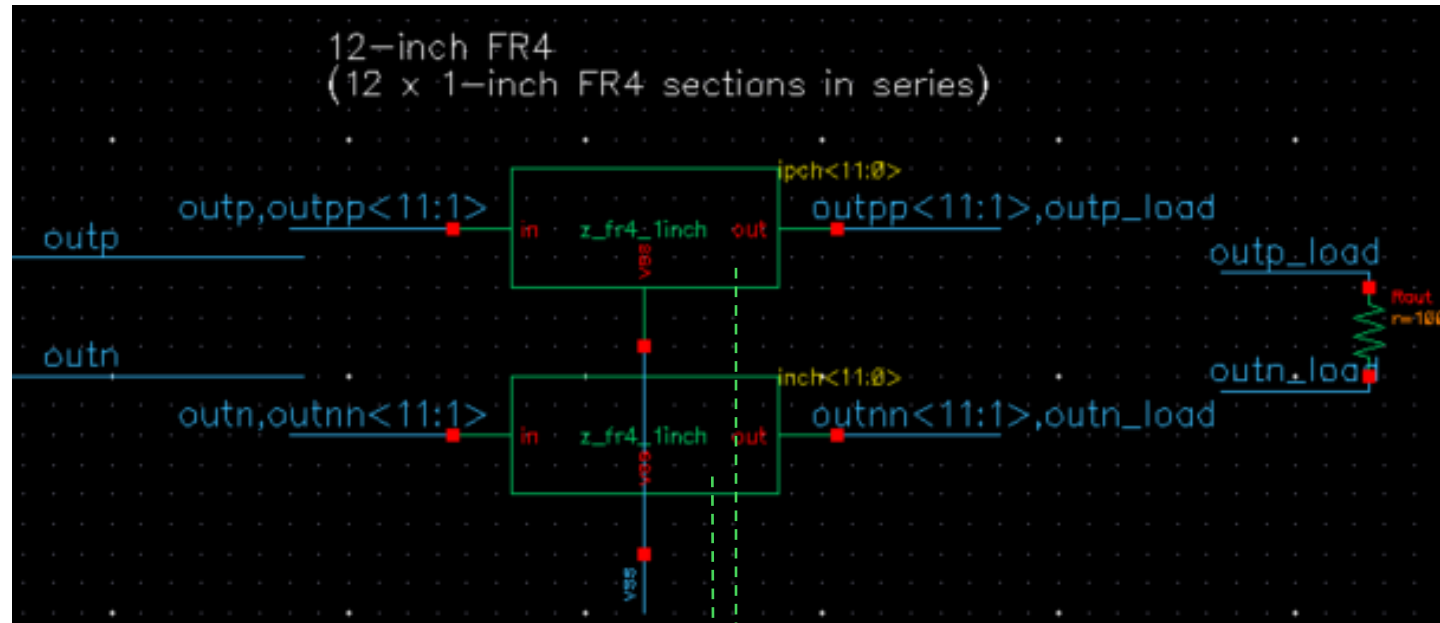

# Simulation Results


## A) Pulse Response: (Without Equalization)

	Pre-Cursor1	Main-Cursor	Post-Cursor1	Post-Cursor2
Adjusted VSWING(PK2PK)	$(18 / 303) * 500 \text{ mV} = 29.7 \text{ mV}$	$(303 / 303) * 500 \text{ mV} = 500 \text{ mV}$	$(88 / 303) * 500 \text{ mV} = 145.2 \text{ mV}$	$(42 / 303) * 500 \text{ mV} = 69.3 \text{ mV}$
Equivalent IBIAS	$29.7 \text{ mV} / 50 \text{ Ohms} = 0.6 \text{ mA}$	$500 \text{ mV} / 50 \text{ Ohms} = 10 \text{ mA}$	$145.2 \text{ mV} / 50 \text{ Ohms} = 2.9 \text{ mA}$	$69.3 \text{ mV} / 50 \text{ Ohms} = 1.4 \text{ mA}$
# of fingers	(m = 12)	(m = 200)	(m = 58)	(m = 28)

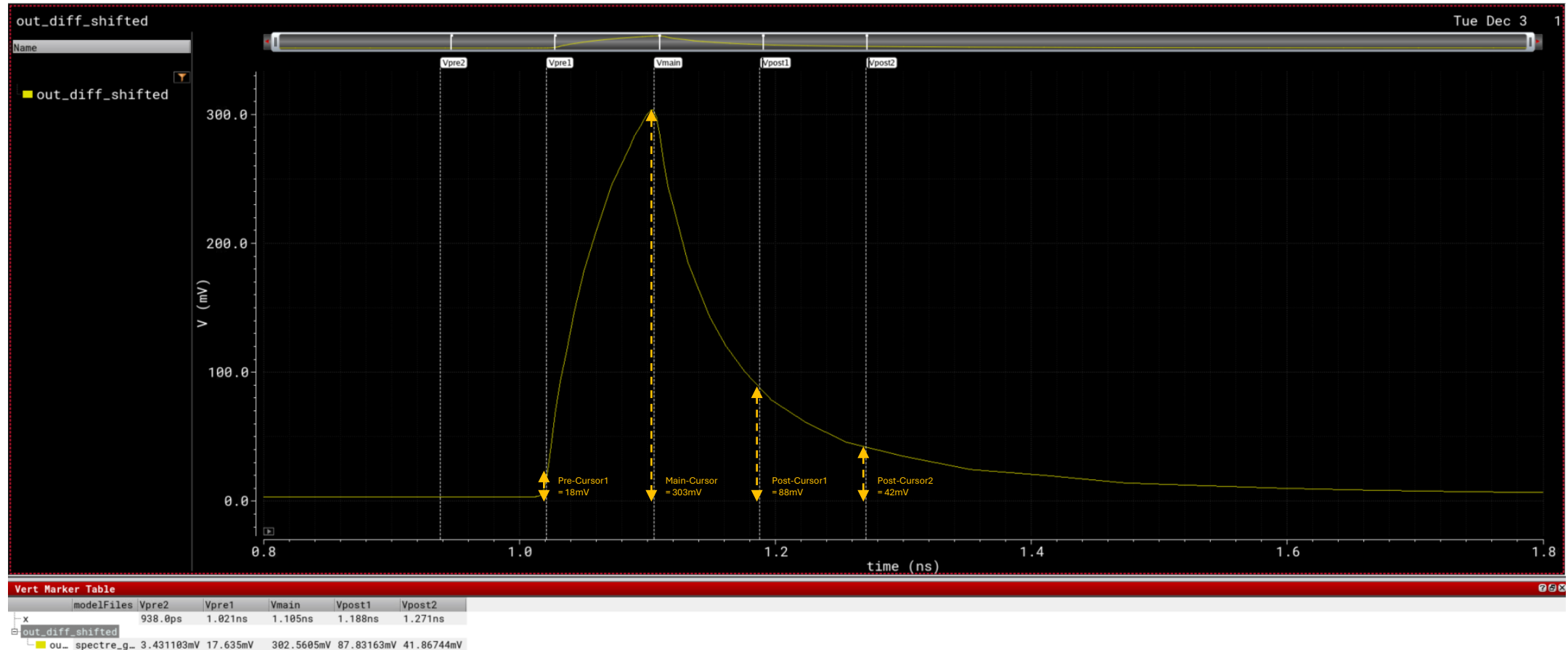


# Simulation Results
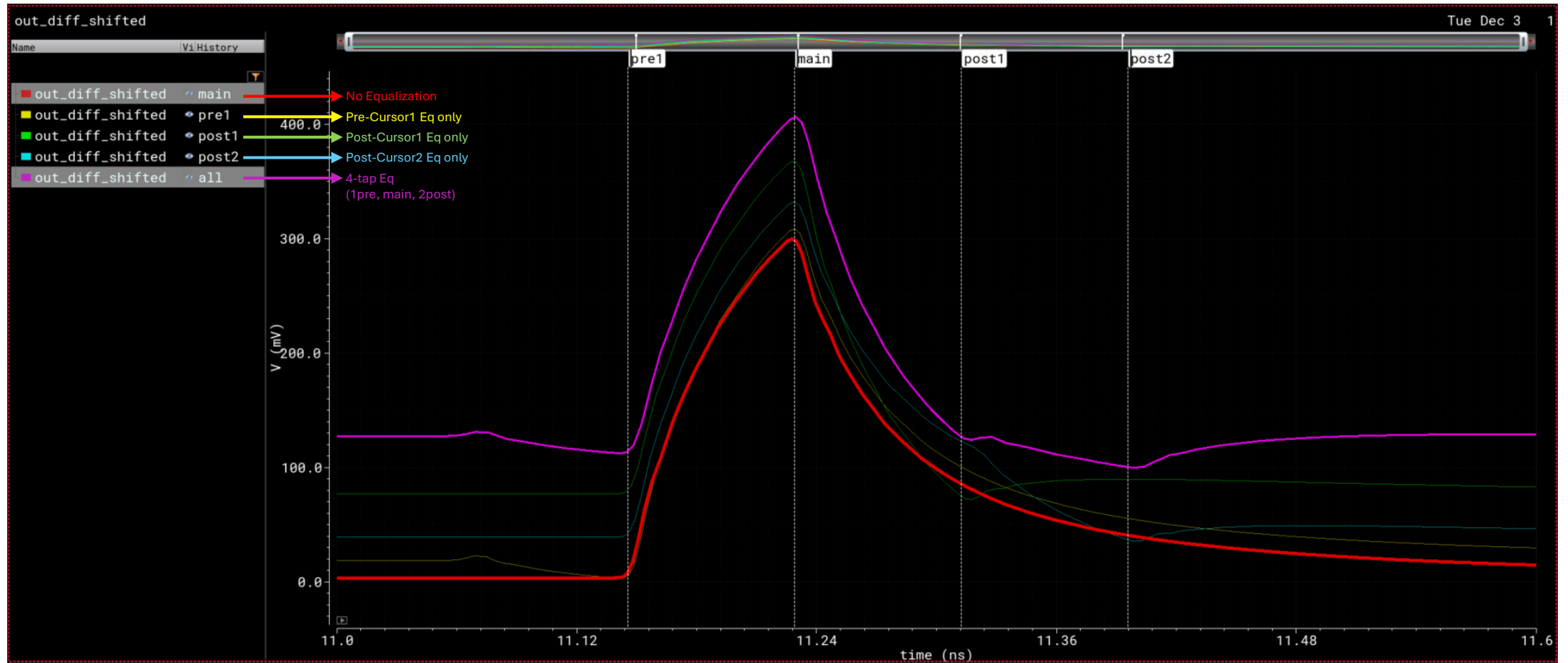
## A) Pulse Response: (With Equalization)




# Simulation Results
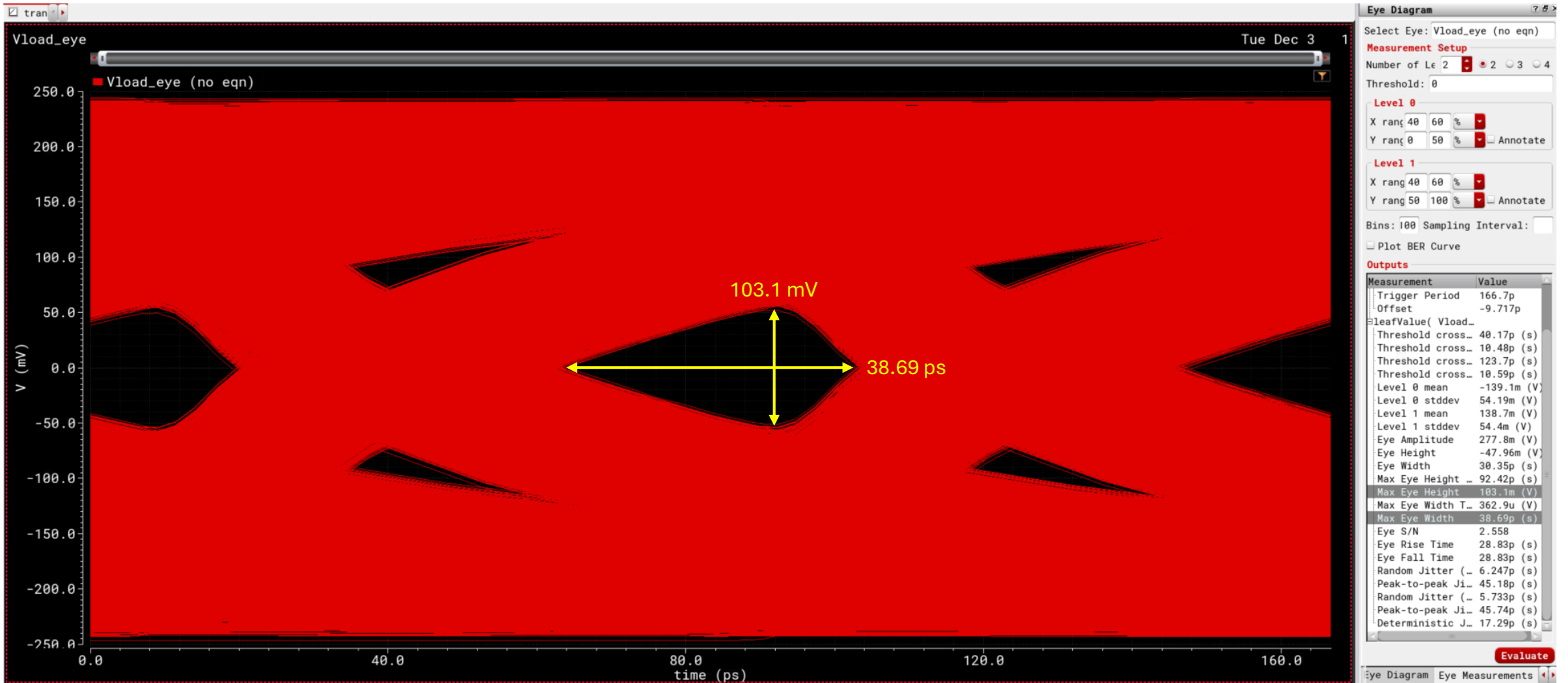
## B) Eye Diagram: (Without Equalization)



# Simulation Results


## B) Eye Diagram: (With Equalization)

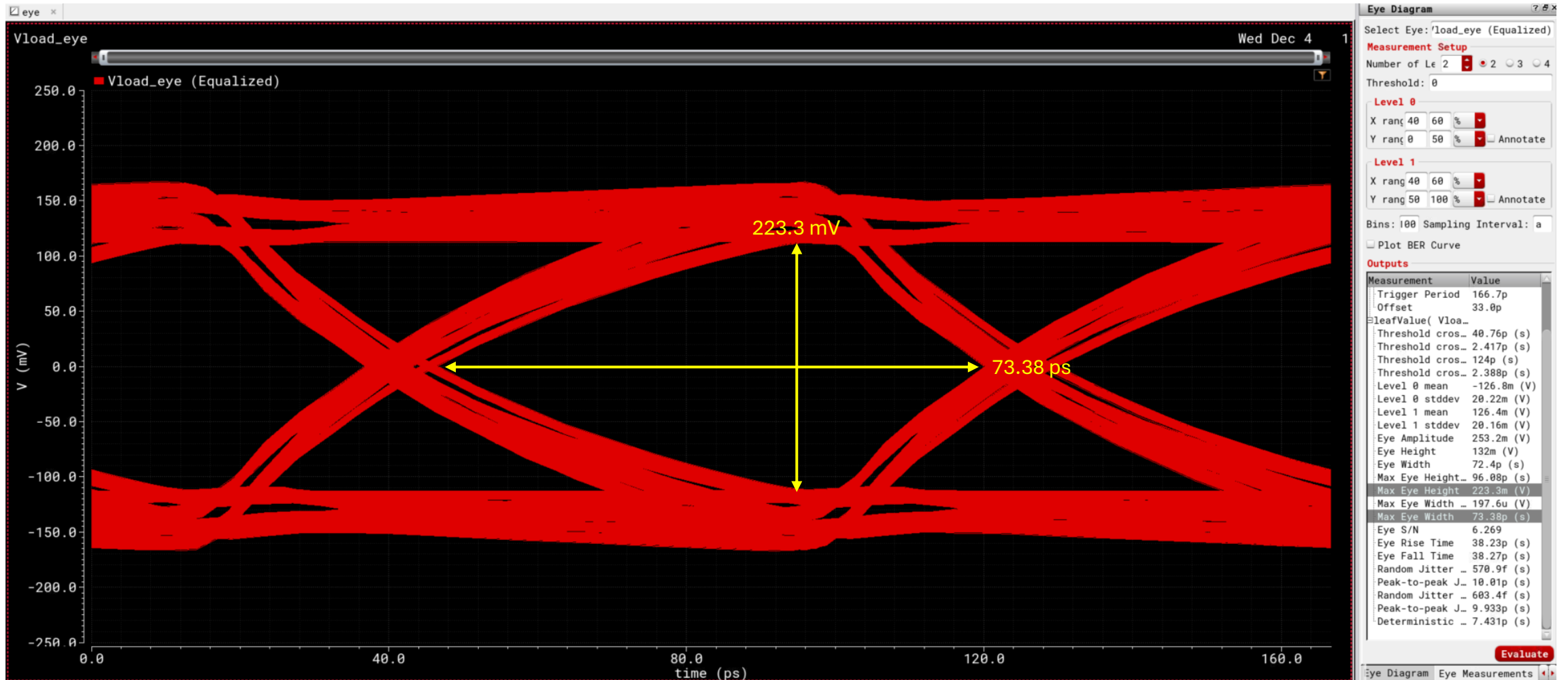

# Simulation Results

## B) Eye Diagram:


	No Equalization	With Equalization (4-tap)
Eye Height (Max)	103.1 mV	223.3 mV
Eye Width (Max)	38.69 ps	73.38 ps
Swing (PK2PK)	500 mV (-250mV ~ +250mV)	328 mV (-164mV ~ +164mV)

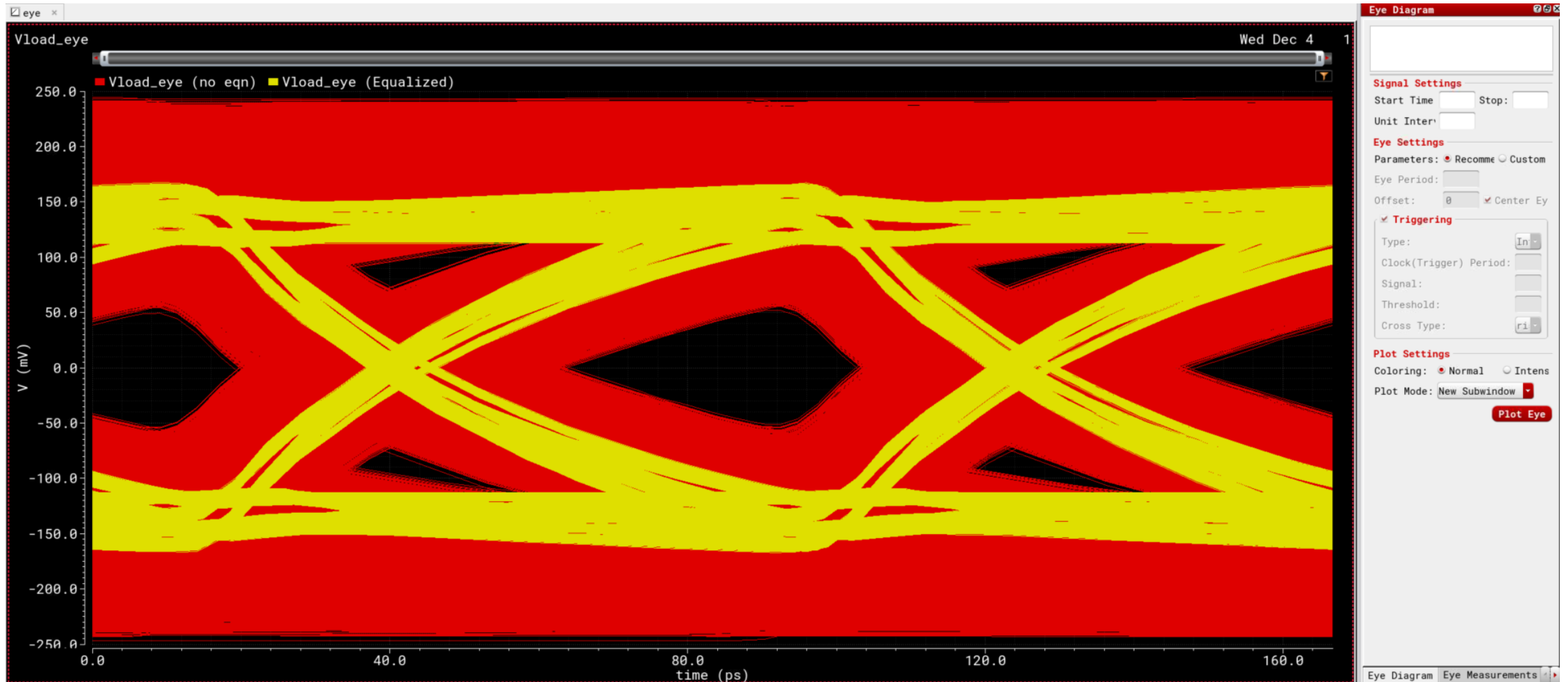




# Simulation Results
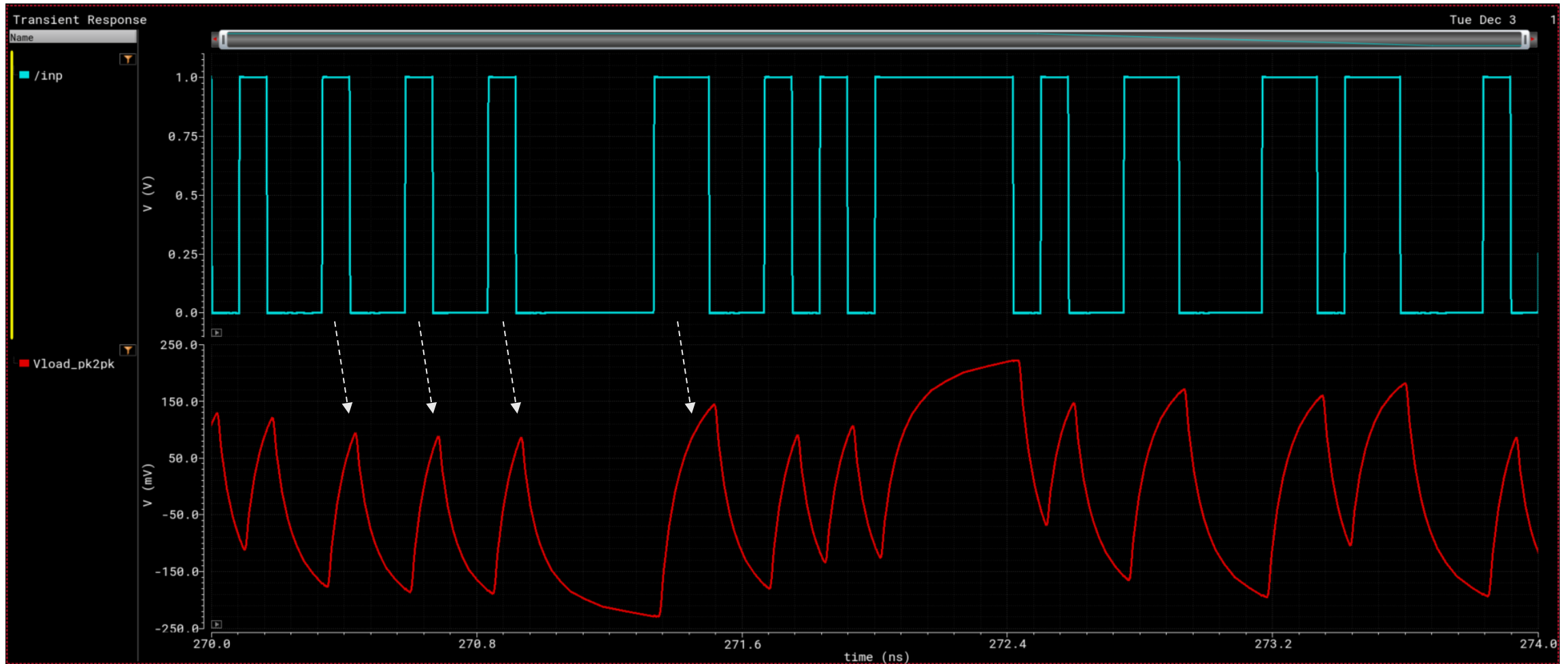
## C) Transient Waveforms: (Without Equalization)




# Simulation Results
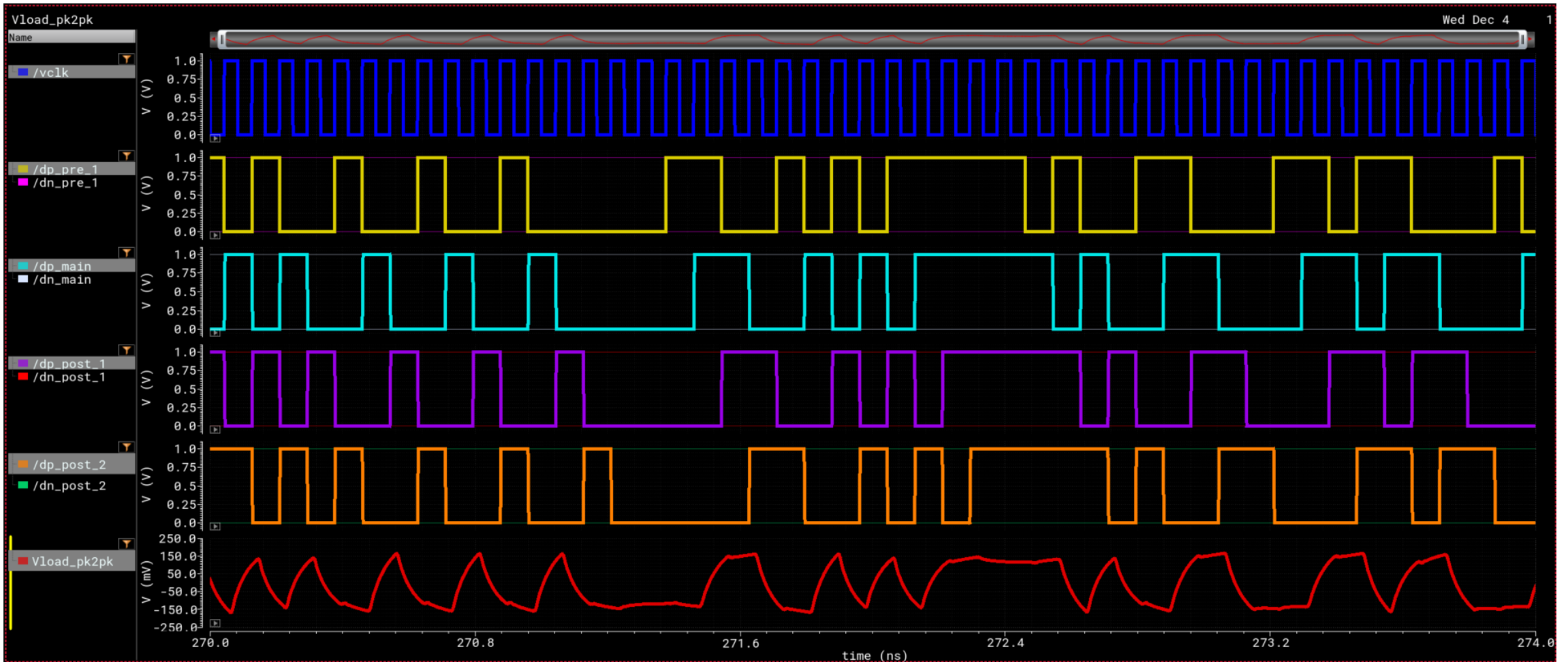
## C) Transient Waveforms: (With Equalization)



# Simulation Results
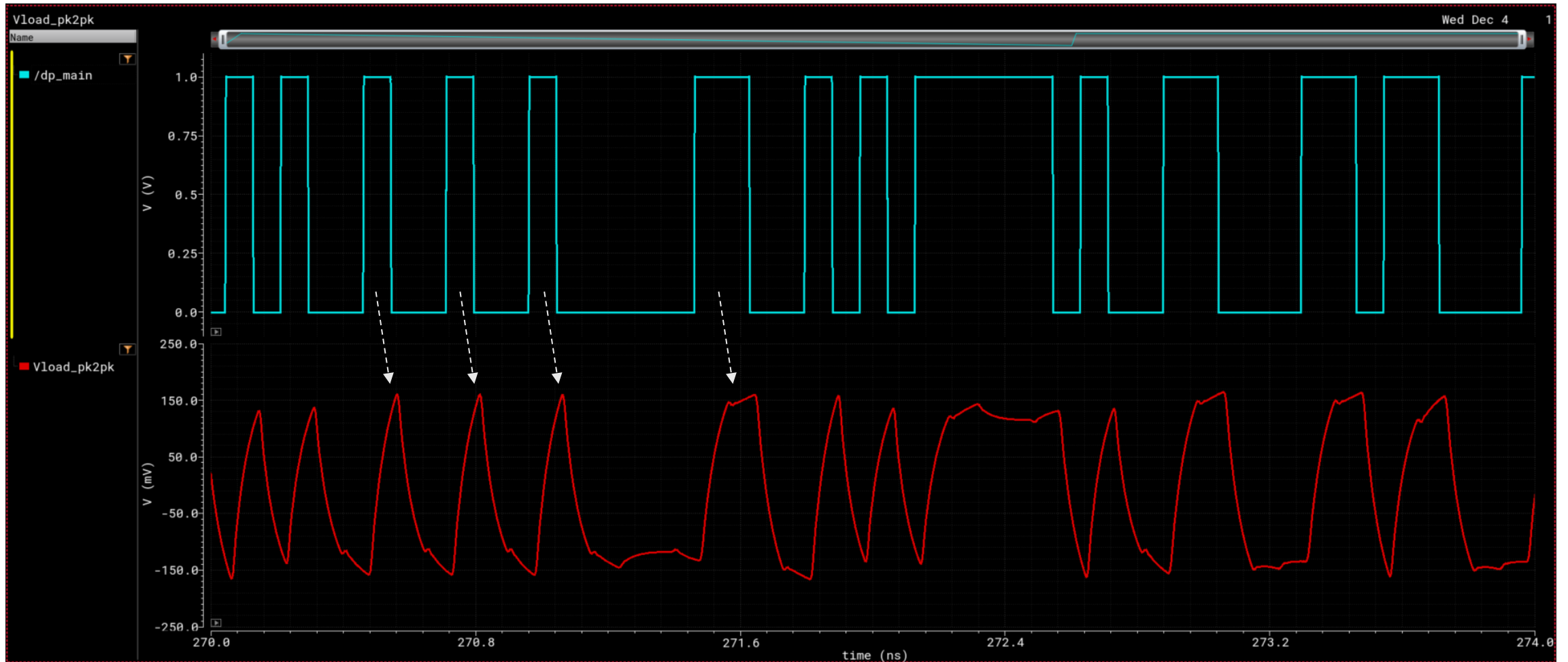
## C) Transient Waveforms: (With Equalization)



# Conclusion

- This project shows the design procedure of a TX FIR Equalizer for a 12 Gb/s input & a channel of 12-inch FR4.
- It also shows how the equalization improves the eye opening of the output, while paying the price of lower swing amplitude & increased latency.